EXP NO: 2 DATE: 10/02/2026

DETERMINATION OF CURRENT IN CIRCUIT USING MESH ANALYSIS.

AIM:

To determine the current in circuit using mesh analysis both theoretically and practically for a given DC circuit.

APPARATUS REQUIRED:

SL. NO.	APPARATUS	SPECIFICATION	QUANTITY
1.	Regulated Power Supply (RPS)	(0 - 30V)	1
2.	Ammeter	(0-10mA) MC	3
3.	Resistors	330Ω, 470Ω, 560Ω	Each 1
4.	Bread board	--	1

CIRCUIT DIAGRAM:

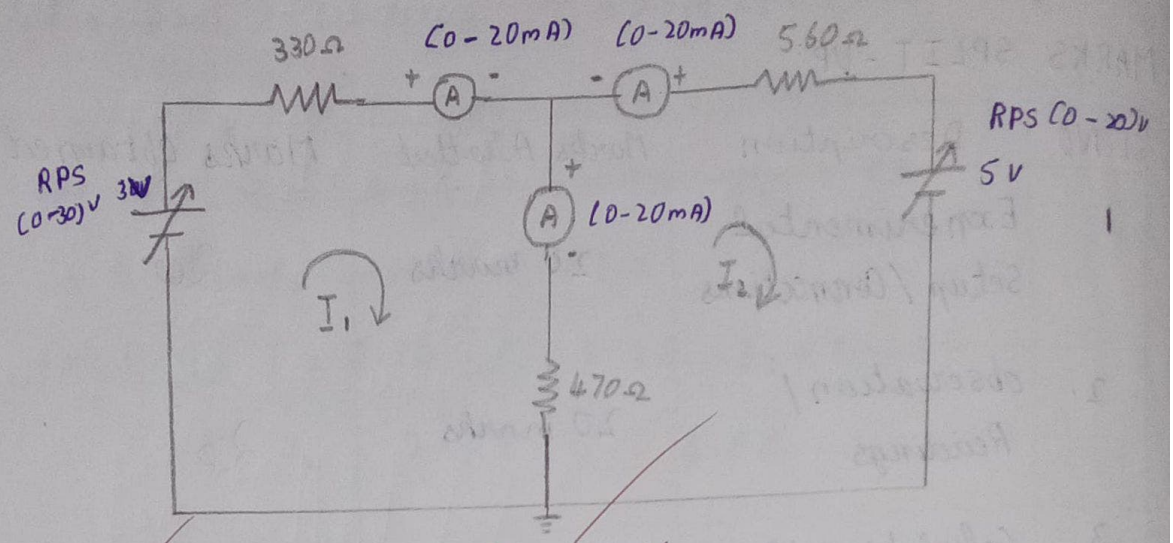

Mesh circuit

TABULAR COLUMN:

Parameters	Theoretical	Practical
I_1	1.2 mA	1.2 mA
I_2	4.23 mA	4.23 mA
$I_1 - I_2$	5.4 mA	5.4 mA

O/P verified
10/12/26

PROCEDURE:

1) Give connections as per the circuit diagram.

2) Switch on the regulated power supply.

3) Note the readings of ammeters and voltmeters and tabulate them.

4) Vary the RPS for different input voltages and note down the readings.

5) Reduce the RPS to its minimum value and switch OFF the supply.

6) Using the tabulated values, verify kirchoff's laws practically, and verify it theoretically.

CALCULATIONS:

THEORITICAL CALCULATIONS:

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$R_{11} = 330\Omega + 470\Omega = 800\Omega$

$R_{12} = 470\Omega$, $R_{21} = 470\Omega$

$R_{22} = 560 + 470 = 1030\Omega$

$$\begin{bmatrix} 800 & -470 \\ -470 & 1030 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 3 \\ -5 \end{bmatrix}$$

$\Delta = 800 \times 1030 - (470)^2$

$= 603100$

$$\Delta_1 = \begin{vmatrix} 3 & -470 \\ -5 & 1030 \end{vmatrix}$$

$= 3090 - 2350 = 740$

$$\Delta_2 = \begin{vmatrix} 800 & 3 \\ -470 & -5 \end{vmatrix} = -4000 + 1410 = -2590$$

$I_1 = \frac{\Delta_1}{\Delta} = \frac{740}{603100} = 1.2mA$

$I_2 = \frac{\Delta_2}{\Delta} = \frac{-2590}{603100} = -4.23mA$

$I_1 - I_2 = 1.2 - (-4.23) = 5.4mA$

MARKS SPLIT-UP:

SI. NO	Description	Marks Allotted	Marks obtained
1	Experimental Setup / Connections	20 marks	20
2.	observation / Readings	20 marks	20
3.	Calculations / Results	20 marks	20
4.	Viva	20 marks	20
5.	Record	20 marks	20
		Total	100

RESULT:

Thus, The Mesh analysis is verified practically and theoretically. The resultant currents for 3/5 V supply are;

100

11/2/21

a) The current across 330Ω resistor is 1.2 mA.

b) The current across 560Ω resistor is -4.23 mA.

c) The current across 470Ω resistor is 5.4 mA.